
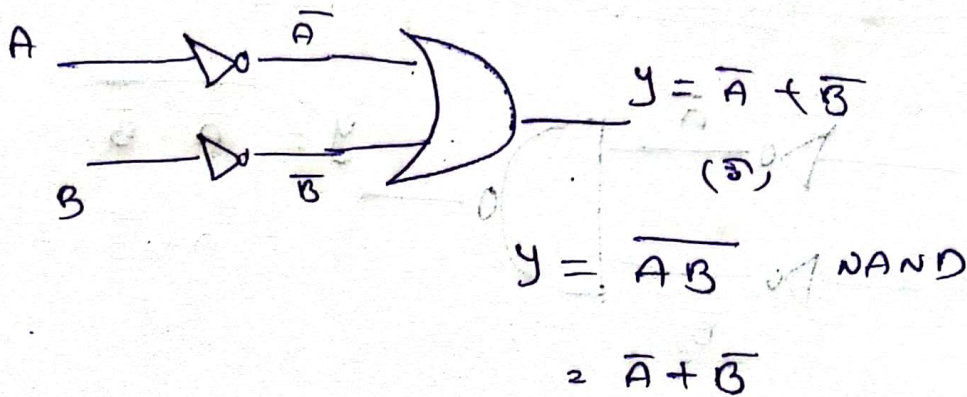


Alternate logic gates (or) Alternate symbols of gates (or) Bubbled gates :-



Bubbled OR gate :-

Bubble indicates "NOT" operation.



OR gate $(y) = A + B$.

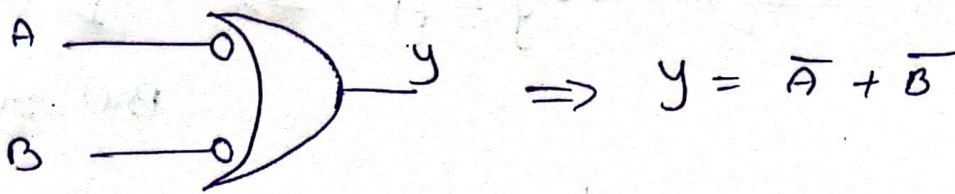

Bubbled AND gate :-

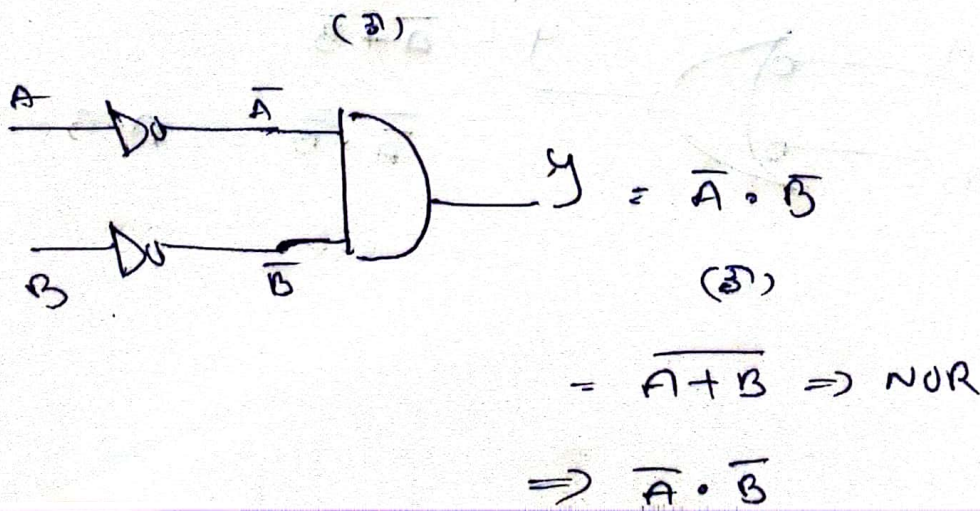
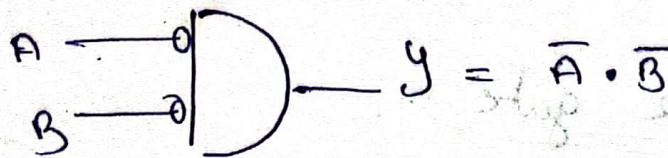


Bubbled NOT gate

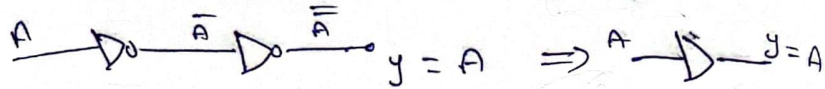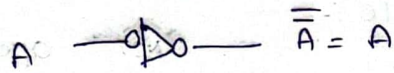


Buffer


Bubbled NAND gate

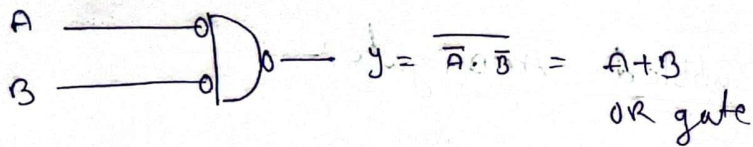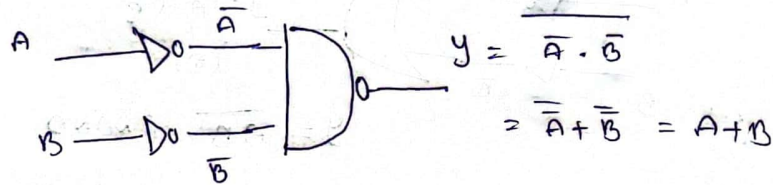

Bubbled NOR gate

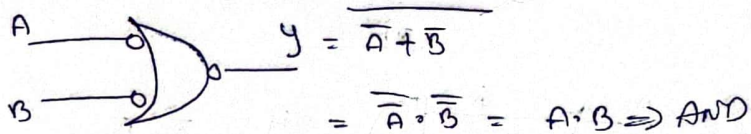


Bubbled X-OR gate

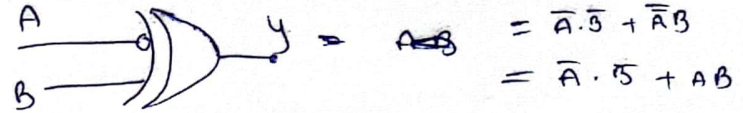


$$y = A \bar{B} + \bar{A} B$$

$$= \bar{A} \cdot B + \bar{A} B$$

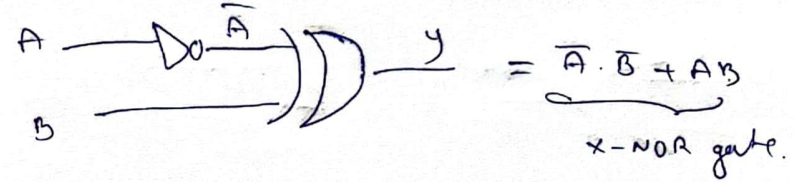

Bubbled X-NOR gate

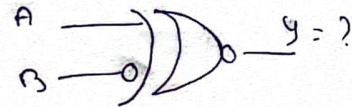


X-NOR

$$A B + \bar{A} \cdot \bar{B}$$

$$y = A \bar{B} + \bar{A} \cdot \bar{B}$$

$$= A \bar{B} + \bar{A} B \Rightarrow \text{X-OR gate}$$

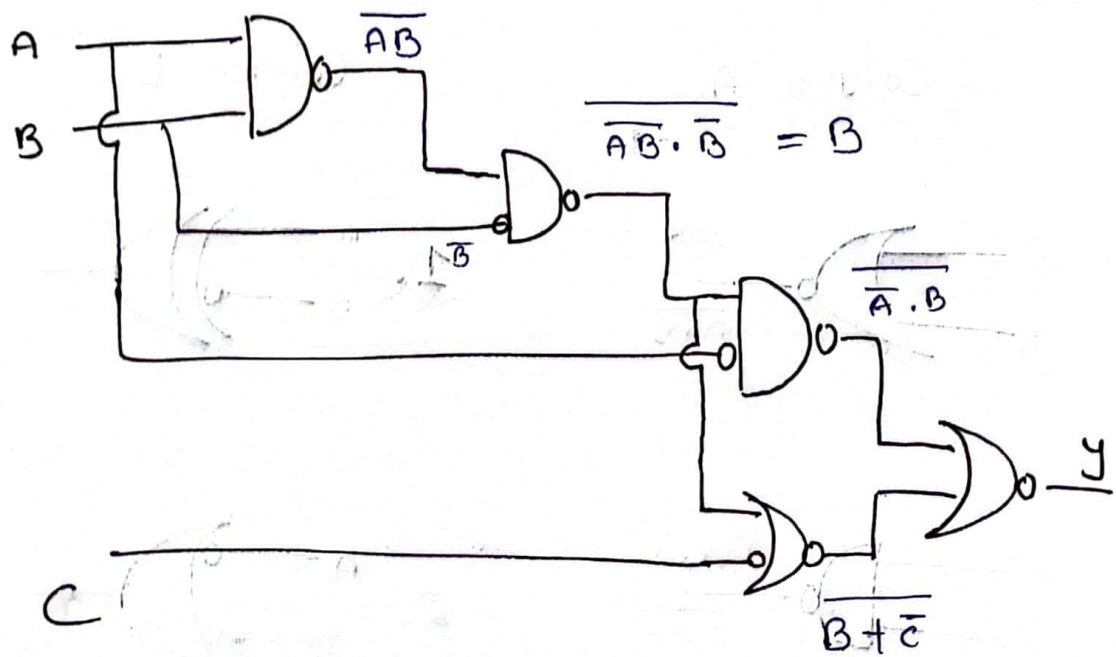(a) The simplified Boolean expression for the g/p y is?



$$\overline{AB \cdot B} \Rightarrow \overline{AB} + \overline{B} = AB + B \Rightarrow B(1+A) \Rightarrow B$$

$$y = \overline{A \cdot B} + \overline{B + C}$$

$$= \overline{A \cdot B} \cdot \overline{B + C} \Rightarrow (\overline{A \cdot B})(B + C)$$

$$= \overline{A} \cdot \frac{B \cdot B}{B} + \overline{A} \cdot B \cdot \overline{C} \Rightarrow \overline{A} \cdot B + \overline{A} \cdot B \cdot \overline{C}$$


$$= B[\overline{A} + \overline{A} \cdot \overline{C}] \Rightarrow B \cdot \overline{A}[1 + \overline{C}]$$

$$y = B \cdot \overline{A}$$


Implement of Boolean fn using logic gates :-

2) $Y = A\bar{B} + \bar{A}B$

using basic gates

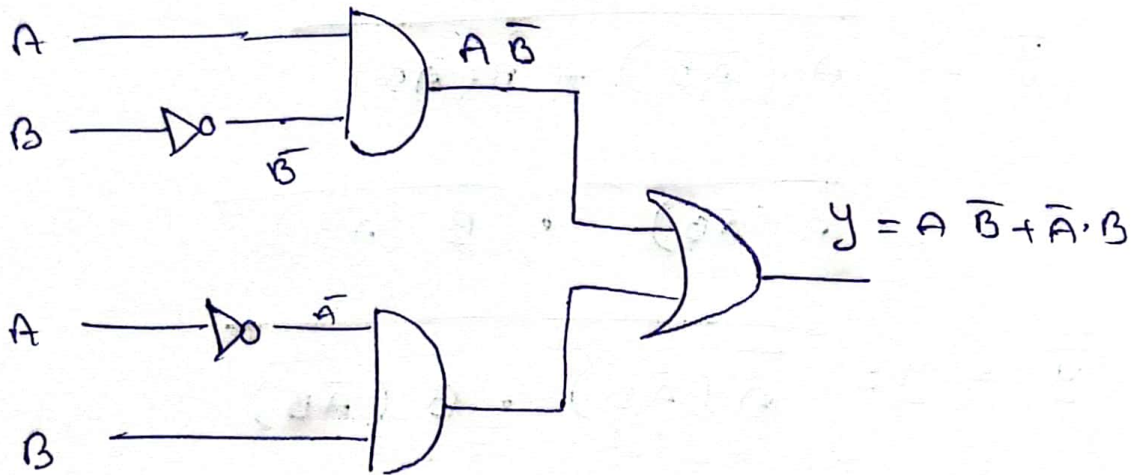

(or)

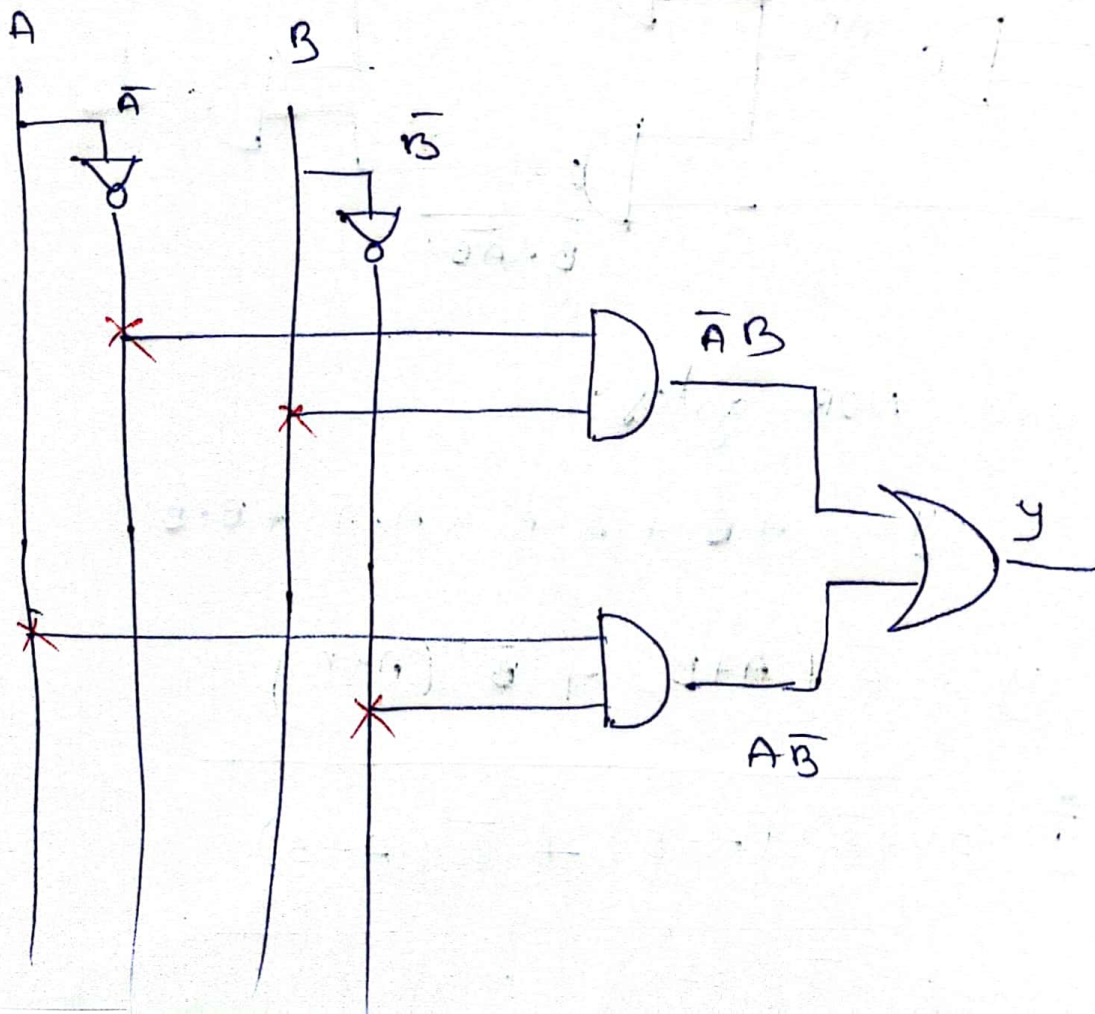

by using NAND gates :-

$$y = A\bar{B} + \bar{A}B + A\bar{A} + B\bar{B}$$


$$= A(\bar{A} + \bar{B}) + B(\bar{A} + \bar{B})$$

$$y = A(\bar{A}\bar{B}) + B(\bar{A}\bar{B})$$

$$\bar{y} = \overline{A(\bar{A}\bar{B}) + B(\bar{A}\bar{B})}$$

$$= \overline{A(\bar{A}\bar{B})} \cdot \overline{B(\bar{A}\bar{B})}$$
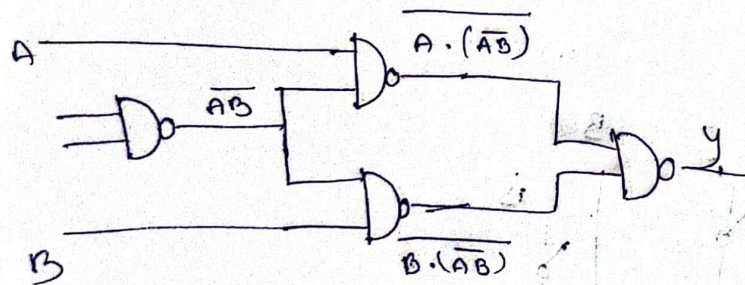
$$\bar{\bar{y}} = y = \overline{A(\bar{A}\bar{B})} \cdot \overline{B(\bar{A}\bar{B})}$$



using NOR gates :-

$$y = A\bar{B} + \bar{A}B + A\bar{A} + B\bar{B}$$

$$y = \bar{A}(A+B) + \bar{B}(A+B)$$


$$\bar{\bar{y}} = \bar{y} = \overline{\bar{A}(A+B) + \bar{B}(A+B)}$$

$$= \overline{\bar{A}(A+B)} \cdot \overline{\bar{B}(A+B)}$$

$$= A + (\bar{A} + \bar{B}) \cdot B + (\bar{A} + \bar{B})$$

$$\bar{y} = y = \overline{[A + (\bar{A} + \bar{B})][B + (\bar{A} + \bar{B})]}$$
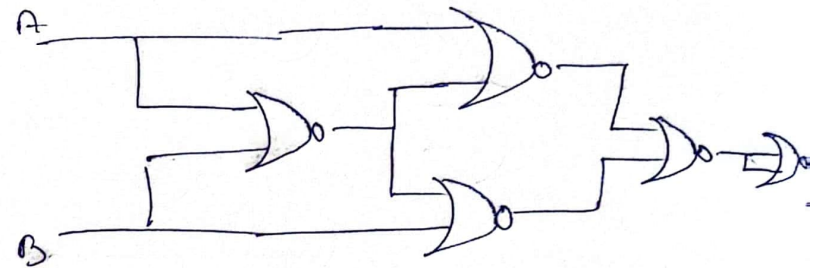
$$= \overline{A + (\bar{A} + \bar{B})} + \overline{B + (\bar{A} + \bar{B})}$$



5 NOR gates